

**General Instructions:** Same as in Homework 1.

**Honor Principle:** For Problem #12, you should work entirely on your own and not discuss with anyone. For Problem #13, the usual honor principle (as in Homework 1) applies.

12. For a string  $x \in \{0, 1\}^*$ , let  $N_1(x)$  denote the number of 1s in  $x$ . The *majority* function  $\text{MAJ}_n : \{0, 1\}^n \rightarrow \{0, 1\}$  is defined as follows:

$$\text{MAJ}_n(x) = \begin{cases} 1, & \text{if } N_1(x) \geq n/2, \\ 0, & \text{otherwise.} \end{cases}$$

Show that  $\text{MAJ}_n$  can be computed using  $O(n)$ -sized circuits. [This is essentially Sipser's Problem 9.26 — if you use the approach suggested in the book, you need to first solve (in sufficient detail) any subproblems that come up, such as Sipser's Problem 9.24.] [2 points]

13. Prove that Shannon's lower bound is tight up to constant factors. That is, improve the upper bound we showed in class by proving that every function  $f : \{0, 1\}^n \rightarrow \{0, 1\}$  has an  $n$ -input circuit of size  $O(2^n/n)$ . [2 points]

The second problem is hard. A hint is to consider the function  $f$  as being  $f(y, z)$ , where  $y = \{x_1, \dots, x_k\}$  and  $z = \{x_{k+1}, \dots, x_n\}$ . Now, the truth table of  $f$  can be viewed as a  $2^k \times 2^{n-k}$  matrix, with the rows indexed by all possible assignments to  $y$ . Each column of this matrix gives us a certain pattern in  $\{0, 1\}^{2^k}$ . What if there aren't too many different patterns? Can we use that fact to cut down on the circuit size?